



HACETTEPE UNIVERSITY
COMPUTER ENGINEERING DEPARTMENT

BM233 LOGIC DESIGN LAB - 2020 FALL

Verilog Project - Resit

February 1, 2021

Student name:
İlayda ATMACA

Student Number:
b21827101

1 Problem Definition

In this experiment, SCP-079 is a microcomputer and at first it was just a student's project. but it gained sentience with time, reached an uncontrollable point, now it has a purpose .SCP-079 needs the attack system in verilog to achieve its malicious goals. and we're designing this verilog. While carrying out this plan, we take our steps by thinking about the possible good and bad scenarios.

2 Draw and include the Mealy state transition diagram

 


Figure 1: Mealy Diagram

3 Verilog code

Include the Verilog code for the system with clear comments and explanations of the code parts.

```
1
2
3  `timescale 1 s / 1s
4
5  module scp_079(input green,input yellow,input red,input clock,
6  output [2:0] state,input [5:0]timer,
7  output reg a1,output reg a2,output reg a3,output reg cheat_out);
8  //a1:attack security output
9  //a2:attack database output
10 //a3:attack control system output
11 reg [2:0]state;
12 reg [2:0]next_state=3'b000;
13
14 parameter s0 =3'b000, s1 = 3'b001 , s2 =3'b010,
15           s3 =3'b011, s4 = 3'b100, s5= 3'b101;
16           //s0:lay low state s1:cheat state s2:attack security state
17           //s3:attack database state s4:fail state s5:connect state
18
19
20 always@(posedge clock)begin
21 state<=next_state;
22 end
23
24 always @(state,red,green,yellow,timer)begin
25 case(state)
26
27 s0:
28 if(red ==1) begin
29 next_state =s1;
30 cheat_out=1;
31 end
32
33 else if(green == 1 && red==0 && yellow==0 && timer>=6'b100011)begin
34 next_state = s2;
35 a1=1 ;
36 end
37
38 else if(yellow == 1 && red==0) begin
39 a1=0;a2=0;a3=0;
40 next_state = s0;
41 end
42
43 s1: if(red ==1 && timer>=6'b011001) begin
44 next_state = s4;
```

```

45 end
46
47 else if(red==0 && timer>=6'b011001)begin
48     next_state = s0;
49     a1=0; a2=0; a3=0;
50     cheat_out=0;
51 end
52
53 s2: if(green == 1 && red==0 && yellow==0 && timer==6'b010100) begin
54     next_state = s3;
55     a2 = 1;
56 end
57 else if(red ==1) begin
58     cheat_out=1;
59     next_state =s1;
60 end
61 else if(yellow ==1 && red==0) begin
62     next_state =s0;
63     a1 =0;
64 end
65
66 s3:
67 if(red==1) begin
68     cheat_out=1;
69     next_state=s1;
70 end
71
72 else if(yellow == 1 && red==0) begin
73     a2 =1;
74     next_state = s2;
75 end
76
77 else if(green == 1 && red==0 && yellow==0 && timer == 6'b001001)begin
78     a3 =1;
79     next_state = s5;
80 end
81 s4:begin end
82
83 s5:begin end
84 default begin a1=0; a2=0; a3=0; cheat_out =0; state = 3'b000; end
85
86 endcase
87 end
88 endmodule

```

```

1
2  `timescale 1 s / 1 s
3  module alloc_tb;
4  reg green;
5  reg yellow;
6  reg red;
7  reg clock;
8  wire [2:0] state;
9  reg [5:0] timer;
10 wire a1;
11 wire a2;
12 wire a3;
13 wire cheat_out;
14
15 //Instantiate scp079
16 scp_079 s(.green(green),.yellow(yellow),.red(red),.clock(clock),.state(state),
17 .a1(a1),.a2(a2),.a3(a3),.timer(timer),.cheat_out(cheat_out));
18
19
20 initial begin
21     green=1;yellow=0;red=0; timer=0;
22     //Initial color situations
23     clock=1;
24     #0.5 clock = 1;
25
26 end
27 //Generate a clock with period
28 always begin clock = ~clock;
29     #0.5;
30 end
31
32 initial begin//Test sequence
33 for(integer i=0;i<35;i=i+1) //state0
34     begin timer=timer+1; #1;end
35
36     timer=0;
37
38 for(integer i=0;i<20;i=i+1)//state2
39     begin timer=timer+1; #1;end
40
41     timer=0;
42 for(integer i=0;i<9;i=i+1)//state3
43     begin timer=timer+1; #1 ; end
44
45 timer=0;
46 for(integer i=0;i<11;i=i+1)//state5
47     begin timer=timer+1;#1;end
48     $finish;

```

```

49 end
50 endmodule

1
2
3
4 module aitrouble_tb;
5
6 initial begin
7
8     green=1;yellow=0;red=0; timer=0;//Initial color situations
9     clock=1;
10    #0.5 clock = 1;
11
12 end
13
14 //Generate a clock with period
15 always begin clock = ~clock;
16     #0.5;
17 end
18
19 initial begin//Test sequence
20 for(integer i=0;i<35;i=i+1) //state0
21     begin timer=timer+1; #1;end
22
23 timer=0;
24 for(integer i=0;i<5;i=i+1)//state2
25     begin timer=timer+1; #1;end
26
27 green=0; red =0; yellow=1;timer=0;
28 for(integer i=0;i<35;i=i+1)//state0
29     begin timer=timer+1; #1 ; end
30
31 green=1; red =0; yellow=0;#1; timer=0;
32
33 for(integer i=0;i<20;i=i+1)//state2
34     begin timer=timer+1;#1;end
35
36 timer=0;
37 for(integer i=0;i<9;i=i+1)//state3
38     begin timer=timer+1; #1 ; end
39
40 timer=0;
41 for(integer i=0;i<8;i=i+1)//state5
42     begin timer=timer+1; #1 ; end
43
44
45 $finish;

```

```

46     end
47 endmodule

1
2
3 module a2trouble_tb;
4
5 initial begin
6     green=1;yellow=0;red=0; timer=0;//Initial color situations
7     clock=1;
8     #0.5 clock = 1;
9
10    end
11
12    //Generate a clock with period
13    always begin clock = ~clock;
14        #0.5;
15    end
16
17    initial begin //Test sequence
18    for(integer i=0;i<35;i=i+1) //state0
19        begin timer=timer+1; #1;end
20        timer=0;
21
22    for(integer i=0;i<20;i=i+1)//state2
23        begin timer=timer+1; #1;end
24
25        timer=0;
26    for(integer i=0;i<5;i=i+1)//state3
27        begin timer=timer+1; #1 ; end
28
29    timer=0;green=0;yellow=1;
30    for(integer i=0;i<35;i=i+1)//state0
31        begin timer=timer+1; #1;end
32
33    green=1;yellow=0; #1;timer=0;
34    for(integer i=0;i<20;i=i+1)//state2
35        begin timer=timer+1; #1;end
36
37        timer=0;
38    for(integer i=0;i<9;i=i+1)//state3
39        begin timer=timer+1; #1 ; end
40
41    timer=0;
42    for(integer i=0;i<4;i=i+1)//state5
43        begin timer=timer+1;#1;end
44
45    $finish;

```

```

46     end
47 endmodule

1
2 module cheatsuccess_tb;
3
4 initial begin
5     green=1;yellow=0;red=0; timer=0;//Initial color situations
6     clock=1;
7     #0.5 clock = 1;
8
9     end
10
11 //Generate a clock with period
12 always begin clock = ~clock;
13     #0.5;
14 end
15
16 initial begin//Test sequence
17 for(integer i=0;i<35;i=i+1) //state0
18     begin timer=timer+1; #1;end
19     timer=0;
20
21 for(integer i=0;i<5;i=i+1)//state2
22     begin timer=timer+1; #1;end
23
24 green=0;yellow=0;red=1; timer=0;
25 for(integer i=0;i<25;i=i+1)begin//state1
26 if(timer==24)begin
27 red=0;
28 end
29 timer=timer+1;#1;end
30
31 green=1;yellow=0;red=0; timer=0;
32 for(integer i=0;i<35;i=i+1)begin//state0
33 if(timer==34)begin
34 green=1;end
35 timer=timer+1;#1;
36 end
37
38 green=1;yellow=0;red=0; timer=0;
39 for(integer i=0;i<20;i=i+1)//state2
40     begin timer=timer+1; #1;end
41     timer=0;
42 for(integer i=0;i<9;i=i+1)//state3
43     begin timer=timer+1; #1;end
44     timer=0;
45 for(integer i=0;i<36;i=i+1)//state5

```



```

46     begin timer=timer+1; #1;end
47
48     $finish;
49 end
50 endmodule

1
2
3 module fail_tb;
4
5 initial begin
6
7     green=1;yellow=0;red=0; timer=0;//Initial color situations
8     clock=1;
9     #0.5 clock = 1;
10 end
11
12 //Generate a clock with period
13 always begin clock = ~clock;
14 #0.5;
15 end
16
17 initial begin//Test sequence
18 for(integer i=0;i<35;i=i+1)//state0
19     begin timer=timer+1; #1;
20     end
21 timer=0;
22 for(integer i=0;i<5;i=i+1)//state2
23     begin timer=timer+1; #1;end
24
25 timer=0;green=0;red=1;
26 for(integer i=0;i<25;i=i+1)//state1
27     begin timer=timer+1; #1 ; end
28
29 timer=0;
30 for(integer i=0;i<12;i=i+1)//state4
31     begin timer=timer+1;#1;end
32
33 $finish;
34 end
35 endmodule

```

4 Waveforms

We did not encounter any danger in this attempt and we realized the plan of SCP-079.

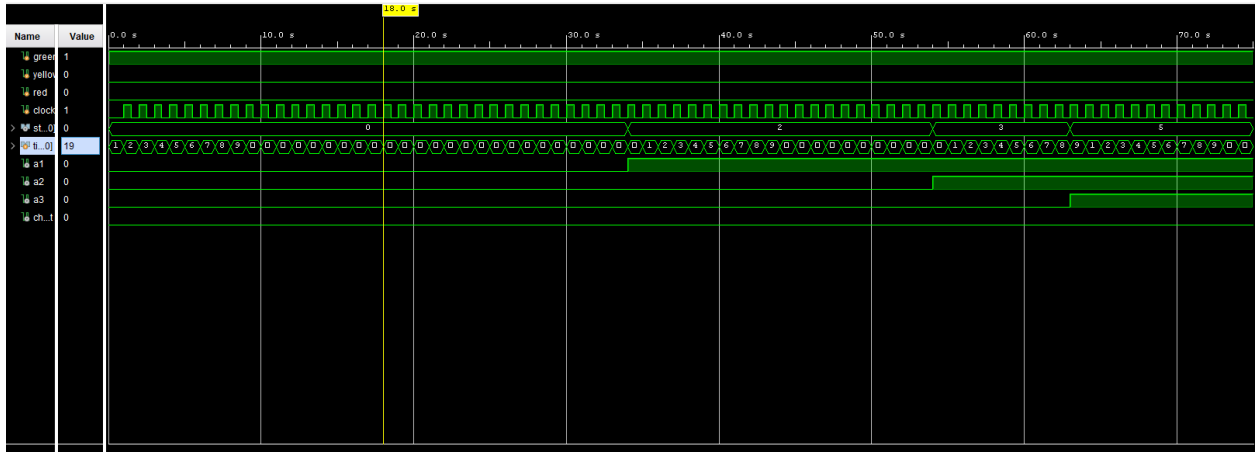


Figure 2: Allok Waveform

We encountered a small danger and the system that we designed reacted to it , but with the measures that we took, our plan was successfully realized.

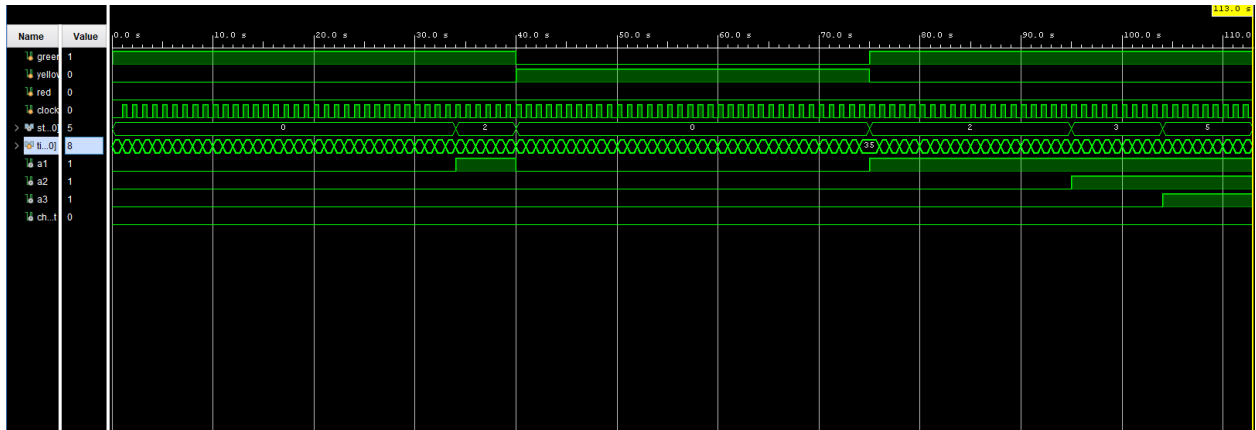


Figure 3: A1trouble Waveform

We encountered more than one danger in this scenario, but we successfully completed this project with our precautions.

 


Figure 4: A2trouble Waveform

this scenario represents a cheat situation. but here we achieved our goal again by being successful

 


Figure 5: Cheatsuccess Waveform

In this scenario, we were unable to overcome the dangers and our plan failed.

 


Figure 6: Fail Waveform

References

- <https://scpcb.gamepedia.com/SCP-079: :text=References-,Description,attempt>